

**CERTIFICATES OF COMPETENCY IN THE MERCHANT NAVY -
MARINE ENGINEER OFFICER**

EXAMINATIONS ADMINISTERED BY THE
SCOTTISH QUALIFICATIONS AUTHORITY
ON BEHALF OF THE
MARITIME AND COASTGUARD AGENCY

STCW 78 as amended CHIEF ENGINEER REG. III/2 (UNLIMITED)

041-33 - ELECTROTECHNOLOGY

THURSDAY, 15 DECEMBER 2016

0915 - 1215 hrs

Examination paper inserts:

--

Notes for the guidance of candidates:

- | |
|---|
| <ol style="list-style-type: none">1. Non-programmable calculators may be used.2. All formulae used must be stated and the method of working and ALL intermediate steps must be made clear in the answer. |
|---|

Materials to be supplied by examination centres:

Candidate's examination workbook Graph paper

ELECTROTECHNOLOGY

Attempt SIX questions only.

All questions carry equal marks.

Marks for each part question are shown in brackets.

1. A non-linear element is connected in series with a resistor across 240 V. d.c. supply.

The non-linear element is governed by the law $I = kV^2$. When the resistor is set to 10Ω the supply current is 12 A.

(a) Calculate EACH of the following:

(i) the resistance value required to reduce the current to 8 A; (8)

(ii) the resistance of the non-linear element when the current is 8 A. (2)

(b) The supply voltage is reduced to 159 V. Calculate the power dissipated in the non-linear element if the series resistor is reset to 10Ω . (6)

2. A 120 μF capacitor is charged through a resistance from a 12 V d.c. supply and the instantaneous charging current at switch-on is 2.55 mA.

(a) Calculate EACH of the following:

(i) the value of the charging resistance; (2)

(ii) the time constant; (2)

(iii) the voltage across the capacitor after 2 s of charging; (3)

(iv) the energy stored after 2 s. (2)

(b) After 2.5 s of charging the supply is switched off and the capacitor is discharged through a $1.2 \text{ k}\Omega$ resistor.

Calculate EACH of the following:

(i) the new time constant; (2)

(ii) the voltage across the capacitor after 124 ms; (3)

(iii) the discharge current at 124 ms. (2)

3. An unregulated d.c. power supply voltage which varies between 10 V and 60 V is connected across a stabiliser circuit comprising a 520 Ω resistor in series with a 8.2 V zener diode. The zener diode has a slope resistance of 12 Ω and requires a minimum operating current of 1 mA. The arrangement supplies a variable load current of 0-40 mA.
- (a) Draw a circuit diagram of the arrangement. (2)
- (b) Calculate EACH of the following:
- (i) the load voltage when the load current is zero and the supply p.d. is 10 V; (4)
- (ii) the load voltage when the load current is 40 mA and the supply p.d. is 50 V; (3)
- (iii) the minimum value of the supply p.d. to give a stabilised load voltage for a load current of 40 mA; (3)
- (iv) the power dissipated in the zener diode when the supply is 60 V and the load current is 30 mA. (4)

4. A series circuit comprising a pure resistor 'R', a coil having resistance and inductance and a capacitor is connected in series across a 60 V variable frequency supply. When the supply frequency is 400 Hz the current reaches its maximum value of 0.8 A and the voltages across the pure resistor 'R' and the capacitor are 40 V and 200 V respectively.

Calculate EACH of the following:

- (a) the value of the pure resistor 'R'; (2)
- (b) the value of the capacitor; (2)
- (c) the resistance and inductance of the coil; (6)
- (d) the p.d. across the coil; (3)
- (e) the coil power factor. (3)

5. (a) State two disadvantages of operating electrical circuits at a low power factor. (2)
- (b) A 3-ph, 440 V, 80 kVA transformer supplies a unity power-factor load of 15 kW and an inductive load of 55 kW and power-factor of 0.67.
- Determine the minimum kVAR rating of a load capacitor bank to ensure that the supply transformer is not overloaded. (10)
- Calculate the current supplied by the transformer in EACH of the following:
- (i) prior to the power factor correction being applied; (2)
- (ii) after the power factor correction is applied. (2)
6. (a) Describe the principle of operation of a 1-ph, a.c. power transformer. (6)
- (b) A 500 kVA power transformer has a full load copper loss of 4 kW and iron loss of 2.5 kW.
- Calculate EACH of the following:
- (i) the kVA load at maximum efficiency; (5)
- (ii) the maximum efficiency for a load power factor of 0.75 lagging at this kVA rating in Q6(b)(i). (5)
7. (a) Explain the reasons for using instrument transformers in a ship's electrical distribution system. (4)
- (b) Sketch a circuit diagram of a voltmeter, an ammeter and a wattmeter connected to a 1-ph, a.c. circuit utilising appropriate current transformers and voltage transformers on a set of a.c. switchboard instruments. (6)
- (c) Explain why the secondary windings of instrument transformers are connected to earth. (4)
- (d) A voltmeter, ammeter and wattmeter, connected to a 1-ph, a.c. circuit, recorded the following readings:
- 440 V, 570 A and 240 kW
- Calculate the power factor of the circuit. (2)

8. (a) State two advantages and two disadvantages of the wound rotor method of starting an induction motor. (4)
- (b) Sketch a circuit diagram showing the rotor/slip rings and starting resistors connection for a three phase wound rotor induction motor. (6)
- (c) A three phase 4 pole wound rotor induction motor has a rotor induced e.m.f. of 230 V, 60 Hz between the slip rings at standstill.
- Calculate EACH of the following:
- (i) the rotor e.m.f. and rotor frequency at a slip of 0.05 p.u.; (4)
- (ii) the synchronous speed. (2)
9. (a) Draw a circuit diagram illustrating how a single thyristor ('silicon controlled rectifier') may be used to provide a variable voltage d.c. output from a single phase a.c. supply. (8)
- (b) Explain how the *firing angle* of the thyristor is varied. (4)
- (c) Sketch waveforms for the output voltage when the firing angle is:
- (i) 60° ; (2)
- (ii) 120° . (2)