

**CERTIFICATES OF COMPETENCY IN THE MERCHANT NAVY –
MARINE ENGINEER OFFICER**

EXAMINATIONS ADMINISTERED BY THE
SCOTTISH QUALIFICATIONS AUTHORITY
ON BEHALF OF THE
MARITIME AND COASTGUARD AGENCY

STCW 95 CHIEF ENGINEER REG. III/2 (UNLIMITED)

041-33 - ELECTROTECHNOLOGY

THURSDAY, PAPER 65

0915 - 1215 hrs

Examination paper inserts:

--

Notes for the guidance of candidates:

- | |
|---|
| <ol style="list-style-type: none">1. Non-programmable calculators may be used.2. All formulae used must be stated and the method of working and ALL intermediate steps must be made clear in the answer. |
|---|

Materials to be supplied by examination centres:

Candidate's examination workbook

ELECTROTECHNOLOGY

Attempt SIX questions only.

All questions carry equal marks.

Marks for each part question are shown in brackets.

1. Fig Q1 shows a measuring circuit in the form of a bridge network. The meter, of resistance $200\ \Omega$, reads $10\ \text{mA}$ in the direction shown.

(a) Calculate the value of the resistance R_X . (8)

(b) The range of the instrument is increased by connecting a resistor of $200\ \Omega$ in parallel with the meter.

Calculate the new reading on the meter. (8)

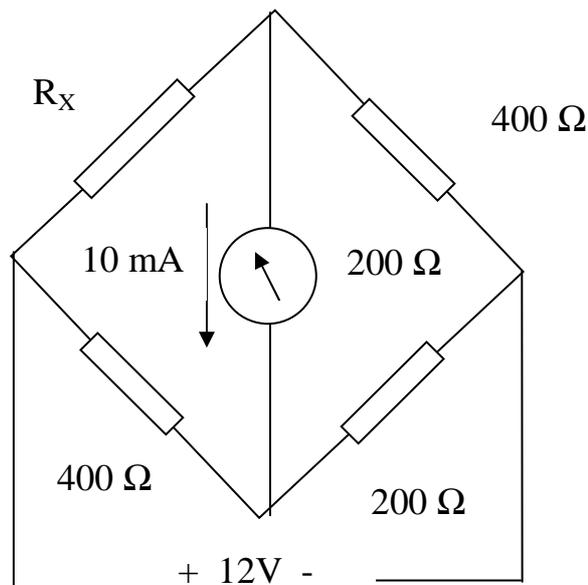


Fig Q1

2. A capacitor of $100\ \mu\text{F}$ is charged for 5 secs from a 100 volt d.c. supply via a resistor of $100\ \text{k}\Omega$.

(a) Calculate EACH of the following:

(i) the voltage across the capacitor at the end of this period; (4)

(ii) the energy stored in the capacitor at the end of this period. (4)

(b) At the end of this period the capacitor is disconnected and a second capacitor of $100\ \mu\text{F}$ already charged to 70 volts is connected in parallel with it.

Calculate EACH of the following:

(i) the final steady state voltage across the pair; (4)

(ii) the energy stored by the pair of capacitors. (4)

3. Fig Q3 shows a basic voltage stabilising circuit using a Zener diode and a series resistor. The Zener diode has a breakdown voltage of 12 V and is rated at 2 W maximum dissipation. The diode requires a minimum reverse current of 2 mA for satisfactory stabilisation and its slope resistance is negligible

Calculate EACH of the following:

(a) the maximum safe input voltage when the output current is zero; (8)

(b) the maximum output current for satisfactory stabilisation when the input voltage is 18 volts. (8)

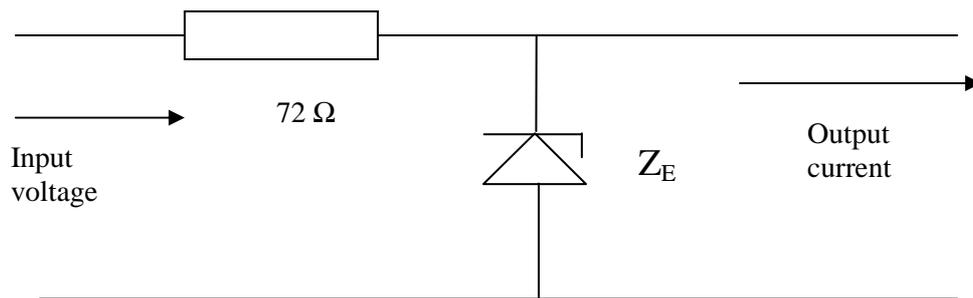


Fig Q3

4. A single phase circuit consists of a capacitor of $50 \mu\text{F}$ in parallel with a coil of unknown resistance and unknown inductance. When connected to 240 V 50 Hz the circuit draws 7 A at power factor 0.8 lag.
- (a) Calculate EACH of the following:
- (i) the resistance of the coil; (5)
 - (ii) the inductance of the coil; (5)
 - (iii) the power factor of the coil. (2)
- (b) Calculate the current drawn if the coil and capacitor are now connected in series to the same supply. (4)
5. A three phase 4 wire unbalanced system has a current in the red phase of 5 A at unity power factor and a current in the yellow phase of 8 A lagging by 30° .
- (a) If the current in the neutral line is 1.93 A in phase with the red line voltage, calculate EACH of the following:
- (i) the magnitude of the current in the blue line; (6)
 - (ii) its angular relationship to the blue line voltage. (6)
- (b) Calculate the total power drawn by this unbalanced circuit, if the value of the phase voltage is 240 V . (4)
6. A four pole three phase induction motor runs off 440 Volt 50 Hz supply. It delivers a shaft output power of 50 kW . The rotational losses (windage and friction) amount to 4 kW and the speed is 24 rev/sec . If the input current is 120 A at a lagging power factor of 0.7 and the stator copper loss is 3 kW , calculate EACH of the following:
- (a) the rotor copper loss; (6)
 - (b) the stator iron loss; (6)
 - (c) the efficiency. (4)
7. (a) Sketch a circuit diagram showing the essential features of a brushless alternator suitable for marine use. (8)
- (b) Explain the function of EACH of the main features sketched in Q7(a). (8)

8. (a) Sketch a circuit diagram showing how a thyristor (silicon controlled rectifier) may be used to vary the d.c. voltage supplied to a load from a single phase a.c. supply. (6)
- (b) Explain the operation of the circuit sketched in Q8(a). (6)
- (c) Sketch the load voltage waveform for EACH of the following delay angles:
- (i) 60° ; (2)
- (ii) 120° . (2)
9. (a) Explain why it is the usual practice to use instrument transformers in a marine distribution system. (4)
- (b) Explain why it may be dangerous to open circuit the secondary winding of a CT (current transformer) whilst operating on load. (4)
- (c) Draw a circuit diagram showing a voltmeter, an ammeter and a wattmeter connected to a single phase power circuit from the same pair of instrument transformers. (5)
- (d) A voltmeter, ammeter and wattmeter connected to a single phase system read 240 V, 70 A and 12.6 kW respectively.
- Determine the load power factor. (3)